



Course Name: Principles of Electrical Engineering II

Course Number and Section: 14:332:222

Lab #1

TA (Instructor): Siwei Mai

Due Date: 2/19/25

Date Submitted: 2/20/25

Submitted by: Chance Reyes cr977

Course Name: Principles of Electrical Engineering II

Course Number and Section: 14:332:222

3.1 Following the discussion in section 7.2 of the textbook, write down the differential equation of the series R-C circuit in the absence of any forcing input. Then, explain or derive equation (1) in your own way.

- $v_c(t) = v_0 e^{-t/RC}$
- If $v_c(0^-) = v_c(0^+)$, then $V_c(0)$ can be substituted with the voltage drop across the resistor R_i in series with V_s . This can be found using the voltage divider formula.

3.2 For $R = 10M\Omega$ and $C = 15\mu F$, determine the expected time constant $\tau = RC$.

- $\tau = RC = 10 \times 10^6 \times 15 \times 10^{-6} = \mathbf{150}$

3.3 Equation (2) for V_{CPP} is rather difficult to prove at this time. Take it as a challenge to derive it as you learn increasingly more on the topic of differential equations.

- We use Euler's identity to represent sin and cos functions with e .

3.4 Explain in your own words why an R-C series circuit can act approximately as an integrator as well as a differentiator and under what conditions

- An R-C series circuit can act as an integrator if the voltage across the capacitor is low compared to the voltage across the resistor by keeping the input Period(T) $<$ the time constant $\tau = RC$.
- An R-C series circuit can also act as a differentiator if the resistance is larger than capacitive reactance.