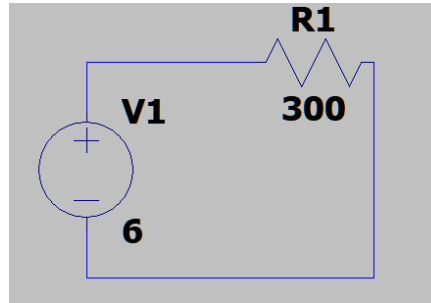


PART C: Pre-Lab


- C.1 Design a circuit with one voltage source of 6V and one resistor such that the current flowing in the circuit is 20mA.



- C.2 For a given resistor, what happens to the voltage drop across that resistor if the current flowing through it is cut in half?

The voltage drop is also cut in half.

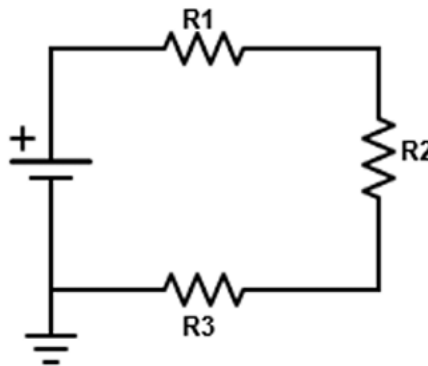- C.3 Assume R1 is 100Ω, R2 is 500Ω, R3 is 1kΩ, and 5V for your power supply.



Calculate the voltage drop across each resistor (V_{R1} , V_{R2} , and V_{R3}) and fill in the Table below.

Voltage	Calculated Voltage Drop
V_{R1}	0.3125
V_{R2}	1.5625
V_{R3}	3.125